



WORKSHEET 2-5 Electrical Symbols

Worksheet Objectives

When you have completed this worksheet, you will be able to:

- Identify electrical symbols used in Toyota wiring diagrams.
- Know where in the EWD manual to find unfamiliar electrical symbols.

Tools and Equipment

For this exercise you will need the following:

- Technician's Handbook
- Pen or pencil
- EWD

Exercise 1: Identifying Electrical Symbols

Use the diagram in Figure 2W5-1 to complete these activities:

- Write the names of the symbols in the blank spaces provided on the diagram.
- Identify whether switch and relay contacts are open or closed. Write your answer on the diagram.
- Fill in the correct term for the question about transistor current.
- Determine whether the crossing wires are connected or not connected. Write your answer on the diagram.

NOTE Use the TIS or the How to Use This Manual section of an electrical wiring diagram book to look up any symbols you do not know.

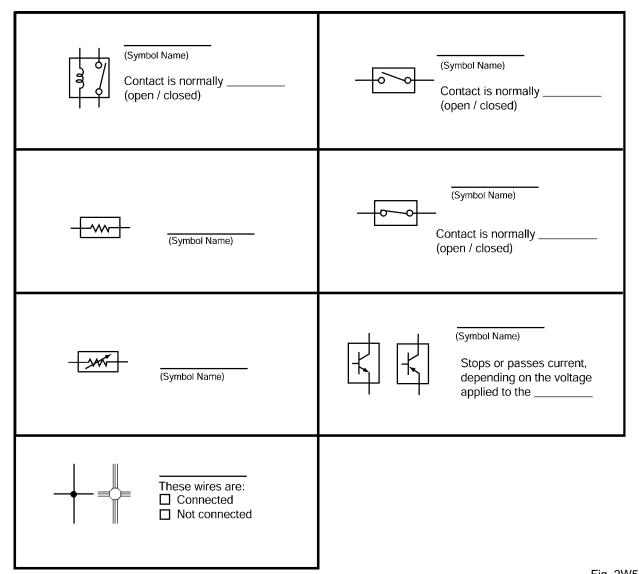


Fig. 2W5-1 TL623f001-2W5

Electrical Symbols

Name:		Date:		
Review this sheet as you are doing the nstructor's presentation and completing copics provided below. Additional space ike you instructor to address. The compuestions, etc.	g the worksheet. is provided und	Ask the insertopic for y	tructor if you have q you to list any other	uestions regarding the concerns that you would
I have questi	ons		I know I can	
Торіс				Comment
Identify Electrical Symbols				

