



## **WORKSHEET 2-7** ***Electrical Wiring Diagrams***

### **Worksheet Objectives**

When you have completed this worksheet, you will be able to:

- Find specific wiring diagrams in the Toyota EWD.
- Determine whether a circuit is source controlled or ground controlled.

### **Tools and Equipment**

For this exercise you will need the following:

- Technician's Handbook
- Pen or pencil
- EWD

### **Exercise 1: Finding Circuit Wiring Diagrams**


Find the following electrical wiring diagrams. Write the page number of the diagram in the first column. Place a check mark beside each one to specify whether it is source or ground controlled.

	Page	Source	Ground
1. Fog Lights			
2. Stop Light			
3. Shift Lock			

# Electrical Wiring Diagrams

Name: \_\_\_\_\_ Date: \_\_\_\_\_

Review this sheet as you are doing the Electrical Wiring Diagrams worksheet. Check each category after viewing the instructor's presentation and completing the worksheet. Ask the instructor if you have questions regarding the topics provided below. Additional space is provided under topic for you to list any other concerns that you would like your instructor to address. The comments section is provided for your personal comments, information, questions, etc.

I have questionsI know I can**Topic****Comment**

Finding Circuit Wiring Diagrams			
Determine if Circuit is Source or Ground Controlled			